

Final Exam
AC Electrical 101+
Part II: Concepts & Three-Phase Electricity

1. Which of the following is (are) NOT a property of three-phase energy distribution systems.

- ☐ a. fewer and smaller conductors than multiple single phase
- ☐ b. induction motors do not require additional starting windings
- ☐ c. motors generate a pulsating torque
- ☐ d. three-phase currents tend to cancel each other

2. Which of the following is technically not a phasor?

- ☐ a. I
- ☐ b. V
- ☐ c. VI
- ☐ d. Z

3. Which of the following represents the "high" or positive polarity?

- ☐ a. arrow tail
- ☐ b. convention
- ☐ c. positive sign
- ☐ d. second letter of double subscript

4. If the maximum sinusoidal voltage is 167.7, what is the rms voltage?

- ☐ a. 115 V
- ☐ b. 120 V
- ☐ c. 220 V
- ☐ d. 240 V

5. What part of the following formula represents the rotating portion of the quantity?


$$v(t) = \text{Re} \left(\left(\frac{169.7\text{V}}{\sqrt{2}} \right) e^{j30^\circ} e^{j\omega t} \right)$$

- ☐ a. $e^{j\omega t}$
- ☐ b. e^{j30°
- ☐ c. Im
- ☐ d. Re

6. A three-phase 208 V (rms) system supplies heating elements connected in a wye configuration. What is the resistance of each element if the total balanced load is 3 kW?

- ☐ a. 4.42 Ω
- ☐ b. 14.42 Ω
- ☐ c. 144.00 Ω
- ☐ d. 1440.00 Ω

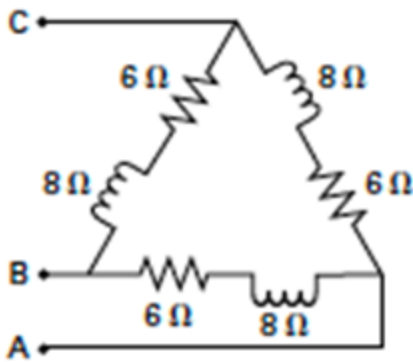7. A three-phase system has a balanced delta load of 5000 kW at 84% power factor. If the line voltage is 4160 V (rms), what is the line current?
- ☐ a. 826 A
 - ☐ b. 941 A
 - ☐ c. 1000 A
 - ☐ d. 1426 A
8. A 120 V (per phase, rms) three-phase system has a balanced load consisting of three $10\ \Omega$ resistances. What total power is dissipated if the connection is a delta configuration?
- ☐ a. 12 W
 - ☐ b. 36 W
 - ☐ c. 1440 W
 - ☐ d. 4320 W
9. A 120 V (per phase, rms) three-phase system has a balanced load consisting of three $10\ \Omega$ resistances. What total power is dissipated if the connection is a wye configuration?
- ☐ a. 12 W
 - ☐ b. 36 W
 - ☐ c. 1440 W
 - ☐ d. 4320 W
10. A balanced delta load consists of three $20\ \Omega\angle 25^\circ$ impedances. The 60 Hz line voltage is 208 V (rms). What is the phase current?
- ☐ a. $10.4\ \text{A}\angle +25^\circ$
 - ☐ b. $10.4\ \text{A}\angle -25^\circ$
 - ☐ c. $6.4\ \text{A}\angle -25^\circ$
 - ☐ d. $12.8\ \text{A}\angle -25^\circ$
11. A balanced delta load consists of three $20\ \Omega\angle 25^\circ$ impedances. The 60 Hz line voltage is 208 V (rms). What is the magnitude of line current?
- ☐ a. 3
 - ☐ b. 10 A
 - ☐ c. 18 A
 - ☐ d. 54 A
12. A balanced delta load consists of three $20\ \Omega\angle 25^\circ$ impedances. The 60 Hz line voltage is 208 V (rms). What is the magnitude of the phase voltage?
- ☐ a. 60 V
 - ☐ b. 120 V
 - ☐ c. 208 V
 - ☐ d. 240 V
13. Three identical impedances are connected in delta across a three-phase system with 240 V (rms) line voltages in an ABC sequence. What is the approximate phase impedance angle?



- ☐ a. 26°
- ☐ b. 36°
- ☐ c. 53°
- ☐ d. 106°

14. A three-phase, 460 V, 100 hp motor has an efficiency of 94% and a power factor of 90%. What is the line current?

- ☐ a. 94 A
- ☐ b. 111 A
- ☐ c. 192 A
- ☐ d. 225 A

15. The per unit of a parameter is the _____ value divided by the _____ value.

- ☐ a. actual / base
- ☐ b. actual / percent
- ☐ c. base / actual
- ☐ d. base / percent

16. Which of the following is one of the usual bases in a per unit system?

- ☐ a. apparent power
- ☐ b. impedance
- ☐ c. line current
- ☐ d. real power

17. A three-phase transformer is rated at 225 kVA with a primary-side voltage of 480 V. The per-unit current in the transformer is 0.4 pu. What is most nearly the actual current?

- ☐ a. 90 A
- ☐ b. 110 A
- ☐ c. 190 A
- ☐ d. 270 A

18. A transformer on the high-voltage side has a voltage of 480 V, an apparent power of 1500 VA, and an impedance of $j50 \Omega$ on the primary side. The turns ratio is 4. What is most nearly the per-unit impedance on the secondary side? [Use the high-voltage side as the base.]


- ☐ a. 0.05 pu
- ☐ b. 0.3 pu
- ☐ c. 0.5 pu
- ☐ d. 50 pu

19. A 240 V (rms) three-phase system drawing 1200 kVA is supplied by a 2400 V (primary-side) transformer bank. Each transformer is connected in a wye-delta (primary-secondary) configuration. What is the approximate ratio of

transformation?

- ☐ a. 0.2
- ☐ b. 2
- ☐ c. 6
- ☐ d. 7

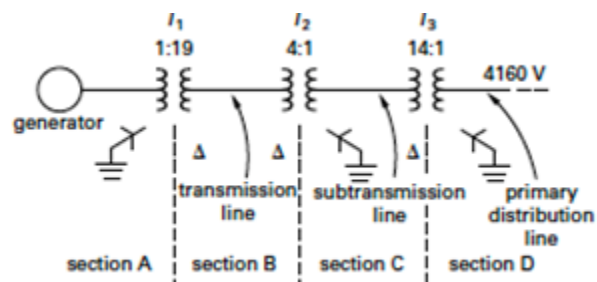20. Consider the one-line diagram of a three-phase distribution system. What is most nearly the generator base voltage?



- ☐ a. 505 V
- ☐ b. 4092 V
- ☐ c. 7080 V
- ☐ d. 12,250 V