

**Final Exam**  
Continuing Education Course #532  
Electrical Power  
Part III: Transformers

1. What term in the transformer model represents the eddy current and hysteresis losses?  
☐ a.  $B_c$   
☐ b.  $G_c$   
☐ c.  $X_p$   
☐ d.  $X_s$
2. What terms represent flux leakage, that is, flux that is NOT mutual?  
☐ a.  $B_c$   
☐ b.  $G_c$   
☐ c.  $X_p$  and  $X_s$   
☐ d.  $X_s$  alone
3. What expression represents the turns ratio,  $a$ , when the turns ratio is defined from the primary to the secondary?  
☐ a.  $I_p / I_s$   
☐ b.  $N_s / N_p$   
☐ c.  $V_p / V_s$   
☐ d.  $\sqrt{Z_s / Z_p}$
4. What type of power is used as a rating for transformers?  
☐ a.  $S$   
☐ b.  $P$   
☐ c.  $Q$   
☐ d. Depends on transformer size
5. What type of loss results from cyclic changes in the magnetic state of the core?  
☐ a. circulating currents  
☐ b. eddy current  
☐ c. hysteresis  
☐ d. reactive
6. A 500 kVA rated, 200 kg iron-core transformer has a coupling coefficient of  $4 \times 10^{-4}$  in a 1.4 T peak magnetic field.  
What is most nearly the eddy current power loss?  
☐ a. 3.0 W  
☐ b. 9.0 W  
☐ c. 400 W  
☐ d. 570 W

7. A 500 kVA rated, 200 kg iron-core transformer has a coupling coefficient of  $4 \times 10^{-4}$  and a Steinmetz exponent in the technical manual of 1.6.

What most nearly is the hysteresis loss?

- ☐ a. 0.1 W
- ☐ b. 6.7 W
- ☐ c. 8.2 W
- ☐ d. 10.1 W

8. A transformer rated operating at 60 Hz is rated at 500 kVA. The core is listed in the data sheets as 200 kg iron, with a coupling coefficient of  $4 \times 10^{-4}$  and a Steinmetz exponent of 1.6 in a 1.4 T peak magnetic field. The primary voltage is 360 kV. The model shows the core resistance as 200 M $\Omega$ .

What most nearly are the total core losses?

- ☐ a. 180 W
- ☐ b. 595 W
- ☐ c. 600 W
- ☐ d. 650 W

9. A transformer is rated for 34.5 kV. The secondary voltage is measured at no load as 35.02 kV.

What is the percent voltage regulation?

- ☐ a. 0.20 %
- ☐ b. 1.4 %
- ☐ c. 1.5 %
- ☐ d. 2.0 %

10. A single-phase transformer rated at 220 V and 0.8 lagging. the primary winding impedance is shown in the data sheet provided as

$$Z_p = R_p + jX_p = 0.012 + j0.020 \text{ pu}$$

What is most nearly the per-unit primary impedance in polar form?

- ☐ a. 0.012 pu  $\angle 62^\circ$
- ☐ b. 0.015 pu  $\angle 62^\circ$
- ☐ c. 0.02 pu  $\angle 62^\circ$
- ☐ d. 0.02 pu  $\angle 59^\circ$


11. When voltage or current ratios are given for a three-phase wye connected transformer, they are assumed to specify what conditions?

- ☐ a. line conditions
- ☐ b. phase conditions
- ☐ c. per the given data sheet
- ☐ d.  $\sqrt{3}$  times line conditions

12. Of the following, which represent the value in a wye connected three-phase transformer?

- ☐ a.  $V_l = V_\phi$
- ☐ b.  $I_l = \sqrt{3} I_\phi$
- ☐ c.  $I_l = \sqrt{3} V_\phi$
- ☐ d.  $I_l = I_\phi$

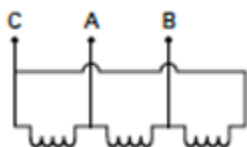13. What of connection does the following represent?



- ☐ a. wye
- ☐ b. delta
- ☐ c. zigzag
- ☐ d. open delta

14. Three-phase delta transformer can lose a single-phase and still provide \_\_\_\_\_ % of their rated load.

- ☐ a. 57.7%
- ☐ b. 66.7%
- ☐ c. 68.6%
- ☐ d. 86.6%

15. A three-phase transformer has an output of 220 V and a current rating of 30 A. The power factor rating is 0.8 lagging.

What is most nearly the total power capability of the transformer?

- ☐ a. 1.4 kW
- ☐ b. 5.2 kW
- ☐ c. 6.6 kW
- ☐ d. 9.1 kW

16. The type of test that determines the core parameters and the turns ratio is the \_\_\_\_\_ test.

- ☐ a. rated power
- ☐ b. short-circuit
- ☐ c. open-circuit
- ☐ d. maximum power

17. A 13.8 kV single-phase transformer is subjected to an open-circuit test with the following results:

$$P_{in} = 900 \text{ W}$$

$$I_{in} = 0.2 \text{ A}$$

$$V_{out} = 460 \text{ V (secondary)}$$

What is the open-circuit conductance,  $G$ ?

- ☐ a. 0.07  $\mu\text{S}$
- ☐ b. 0.96  $\mu\text{S}$
- ☐ c. 1.96  $\mu\text{S}$
- ☐ d. 4.73  $\mu\text{S}$

18. A 13.8 kV single-phase transformer is subjected to an open-circuit test with the following results:

$$P_{in} = 900 \text{ W}$$

$$I_{in} = 0.2 \text{ A}$$

$$V_{out} = 460 \text{ V (secondary)}$$

What is the reactive power,  $Q$ ?

- ☐ a. 898 VAR
- ☐ b. 1123 VAR
- ☐ c. 2609 VAR
- ☐ d. 2903 VAR

19. A 13.8 kV single-phase transformer is subjected to an open-circuit test with the following results:

$$P_{\text{in}} = 900 \text{ W}$$

$$I_{\text{in}} = 0.2 \text{ A}$$

$$V_{\text{out}} = 460 \text{ V (secondary)}$$

What is most nearly the magnitude of the susceptance,  $B$ ?

- ☐ a. 2.0  $\mu\text{S}$
- ☐ b. 4.0  $\mu\text{S}$
- ☐ c. 9.0  $\mu\text{S}$
- ☐ d. 13.7  $\mu\text{S}$

20. A 13.8 kV single-phase transformer is subjected to an open-circuit test with the following results:

$$P_{\text{in}} = 900 \text{ W}$$

$$I_{\text{in}} = 0.2 \text{ A}$$

$$V_{\text{out}} = 460 \text{ V (secondary)}$$

What is most nearly the turns ratio,  $a$ ?

- ☐ a. 0.03
- ☐ b. 0.07
- ☐ c. 30
- ☐ d. 414

21. A 32 kVA single-phase transformer is rated at 15 kV on the primary. A 60 Hz short-circuit test on the primary resulted in the following reported values.

$$P_{\text{in}} = 1 \text{ kW}$$

$$I_{\text{in}} = 20 \text{ A}$$

$$I_s = 100 \text{ A}$$

$$V_p = 80 \text{ V}$$

Noting that  $I_{\text{in}} = I_p = I_{1\text{sc}}$  and  $P_{\text{in}} = P_{\text{sc}}$  will aid in the solution. The transformer is designed for maximum efficiency meaning  $R_p = a^2 R_s$ .

What is the primary resistance?

- ☐ a. 0.05  $\Omega$
- ☐ b. 1.25  $\Omega$
- ☐ c. 2.25  $\Omega$
- ☐ d. 2.50  $\Omega$

22. A 32 kVA single-phase transformer is rated at 15 kV on the primary. A 60 Hz short-circuit test on the primary resulted in the following reported values.

$$P_{\text{in}} = 1 \text{ kW}$$

$$I_{\text{in}} = 20 \text{ A}$$

$$I_s = 100 \text{ A}$$

$$V_p = 80 \text{ V}$$

Noting that  $I_{\text{in}} = I_p = I_{1\text{sc}}$  and  $P_{\text{in}} = P_{\text{sc}}$  will aid in the solution. The transformer is designed for maximum efficiency meaning  $R_p = a^2 R_s$ .

What is the turns ratio?

- ☐ a. 0.05
- ☐ b. 0.25
- ☐ c. 0.5
- ☐ d. 5

23. A short-circuit test is conducted on a transformer rated at 15 kVA and 1200 primary volts.

What is the value of the input current,  $I_{1\text{sc}}$ ?

- ☐ a. 1.25 A
- ☐ b. 11.5 A
- ☐ c. 12.0 A
- ☐ d. 12.5 A

24. What two parameters from the ABCD scheme are associated with the output voltage.

- ☐ a. A and B
- ☐ b. A and C
- ☐ c. B and C
- ☐ d. B and D

25. What type of transformer is used to control the voltage or phase angle is both?

- ☐ a. Distribution
- ☐ b. Instrument
- ☐ c. Power
- ☐ d. Regulating